

1. Download and install *Digital* from  
<https://github.com/hneemann/Digital>
2. Run *bin2hex.cir* to see how a hexadecimal display works. Especially observe the use of the *Input* component for changing the values of the display input bits.
3. Modify the circuit so that the seven-segment shows the summation of two 3-bit numbers. There is an *adder* under

Components -> Arithmetic

menu of *Digital*. Modify the adder for an appropriate number of input bits. The numbers will be input by the use of two sets of three *Input* components. *Input* is available at

Components -> IO -> Input

**Submit:**

1. A screenshot of your simulation showing the result of  $7 + 4$ .
2. Your *Digital* simulation file (with .cir extension).

□